

CPLD MAX3000A

Counters in VHDL

10th April, 2023

VHDL Programming and CPLD Application the VHDL codes.

Components used:

Quartus software,CPLD Board and USB connector

Summary of the Experiment:

Using Quartus application to write the VHDL code for the given problems and dump the code the CPLD(blue board).

Truth Table(s):

1. Asynchronous up counter

<i>Reset</i>	<i>Clock</i>	<i>Q_(t-1)</i>	<i>Q_(t)</i>
1	X	X	000
0	↓	000	001
0	↓	001	010
0	↓	010	011
0	↓	011	100
0	↓	100	101
0	↓	101	110
0	↓	110	111
0	↓	111	000

Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;



entity q1 is
Port ( CLOCK : in STD_LOGIC;
RESET : in STD_LOGIC;
Q : out STD_LOGIC_VECTOR (2 downto 0));
end q1;

architecture Behavioral of q1 is
signal q_tmp: std_logic_vector(2 downto 0):= "000";
begin
process(CLOCK,RESET)
```

```

begin
  if RESET = '1' then
    q_tmp <= "000";
  1
  elsif
    falling_edge(CLOCK)
  then
    if(q_tmp(0)='0')
  then
    q_tmp(0)<='1';
    elsif q_tmp(1)='0'
  then q_tmp(1)<= '1';
    q_tmp(0)<='0';
    elsif q_tmp(2)= '0'
  then q_tmp(2)<= '1';
    q_tmp(1)<= '0';
    q_tmp(0)<='0';
    else
    q_tmp(2)<= '0';
    q_tmp(1)<= '0';
    q_tmp(0)<='0';
    end if;
  end if;
  end process;
  Q <= q_tmp;
end Behavioral;

```

 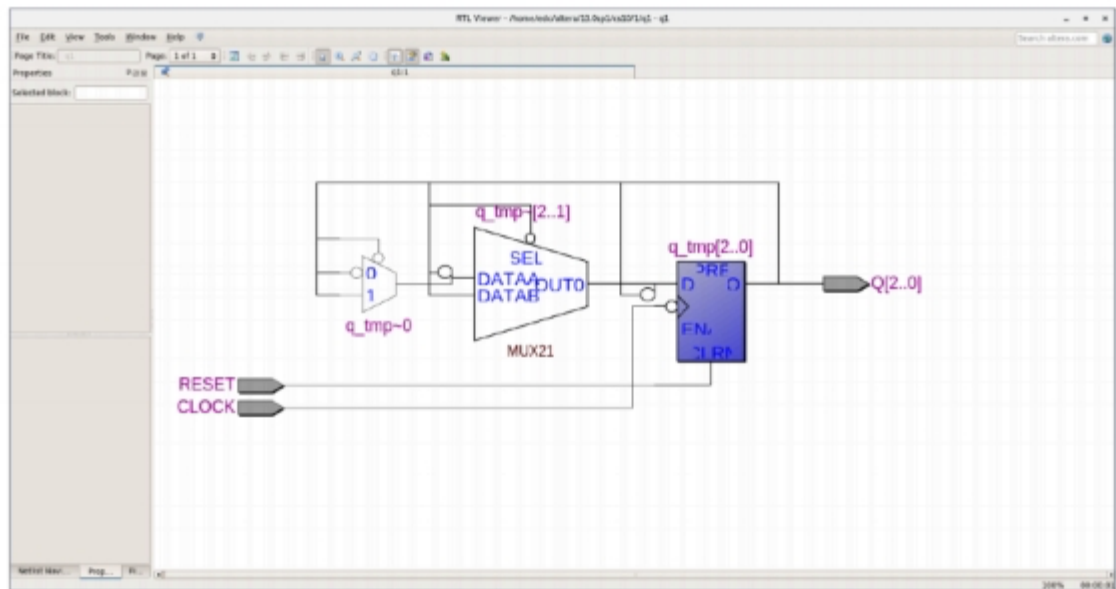

2. Asynchronous Down Counter

$Reset$	$Clock$	$Q_{(t-1)}$	$Q_{(t)}$
1	X	X	111
0	↓	111	110
0	↓	110	101
0	↓	101	100
0	↓	100	011
0	↓	011	010
0	↓	010	001
0	↓	001	000
0	↓	000	111

code :

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

entity q2 is

```
Port ( CLOCK : in STD_LOGIC;  
RESET : in STD_LOGIC;  
Q : out STD_LOGIC_VECTOR (2 downto 0));  
end q2;
```

architecture Behavioral of q2 is

```
signal q_tmp: std_logic_vector(2 downto 0):= "111";
```

```
begin
```

```
process(CLOCK,RESET)
```

```
begin
```

```
if RESET = '1' then
```

```
    q_tmp <= "000";
```

```
elsif falling_edge(CLOCK) then
```

```
    if(q_tmp(0)='1') then
```

```
        q_tmp(0)<='0';
```

```
    elsif q_tmp(1)='1' then
```

```
        q_tmp(1)<='0';
```

```
        q_tmp(0)<='1';
```

```
    elsif q_tmp(2)='1' then
```

```
        q_tmp(2)<='0';
```

```
        q_tmp(1)<='1';
```

```
    3
```

```
        q_tmp(0)<='1';
```

```
    else
```


```
        q_tmp(2)<='1';
```

```
        q_tmp(1)<='1';
```

```

        q_tmp(0) <= '1';
    end if;
end if;
end process;
Q <= q_tmp;
end Behavioral;

```

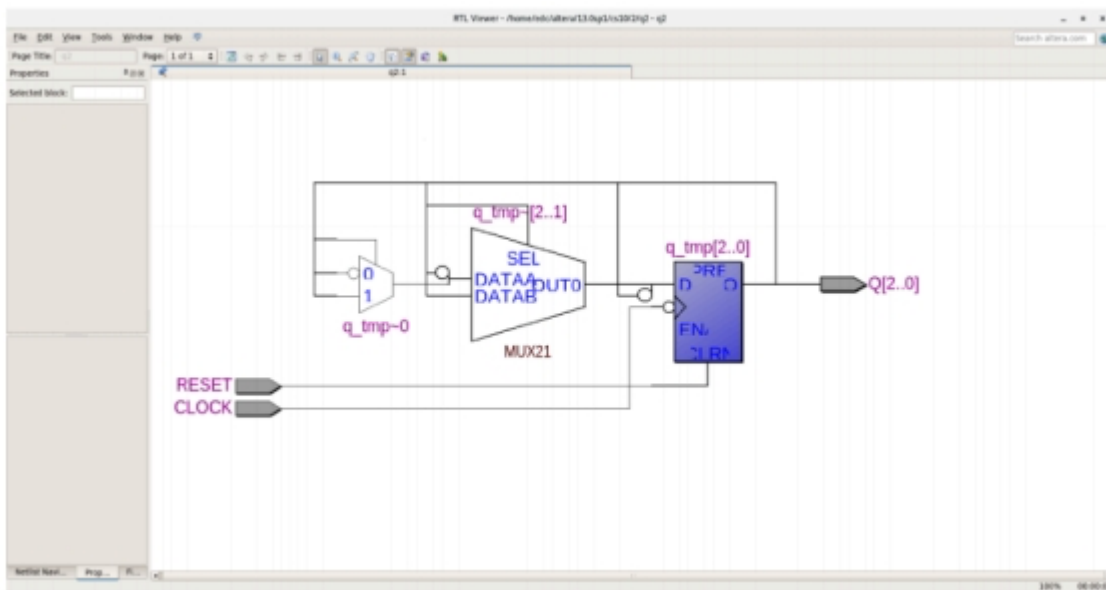

Circuit Snapshots:



3. Sequence Counter

<i>Reset</i>	<i>Clock</i>	$Q_{(t-1)}$	$Q_{(t)}$
1	X	X	011
0	↓	011	000
0	↓	000	010
0	↓	010	101
0	↓	101	001
0	↓	001	100
0	↓	100	011

code :

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

entity **q3** is

```
port (clk, reset: in std_logic;
```

```
q: out std_logic_vector (2 downto 0));
```

```
end q3;
```

architecture **two_seg_arch** of **q3** is

```
signal r_reg: std_logic_vector (2 downto 0);
```

```
signal r_next: std_logic_vector (2 downto 0);
```

```
Begin
```

```
-- register
```

```
process (clk, reset)
```

```
begin
```

```
if (reset= '1') then
```

```
    r_reg <= "011";
```

```
    elsif falling_edge(clk) then
```

```
        r_reg <= r_next;
```

```
    end if;
```


```
end process;
```


```
-- next-state logic
```

```

r_next <= "011" when
r_reg="100" else
"000" when r_reg="011"
else
"010" when r_reg="000"
else
"101" when r_reg="010"
else
"001" when r_reg="101"
else
"100" when r_reg="001"
else
"011"; -- r_reg="111"
-- output logic
q <= r_next;
end two_seg_arch;

```

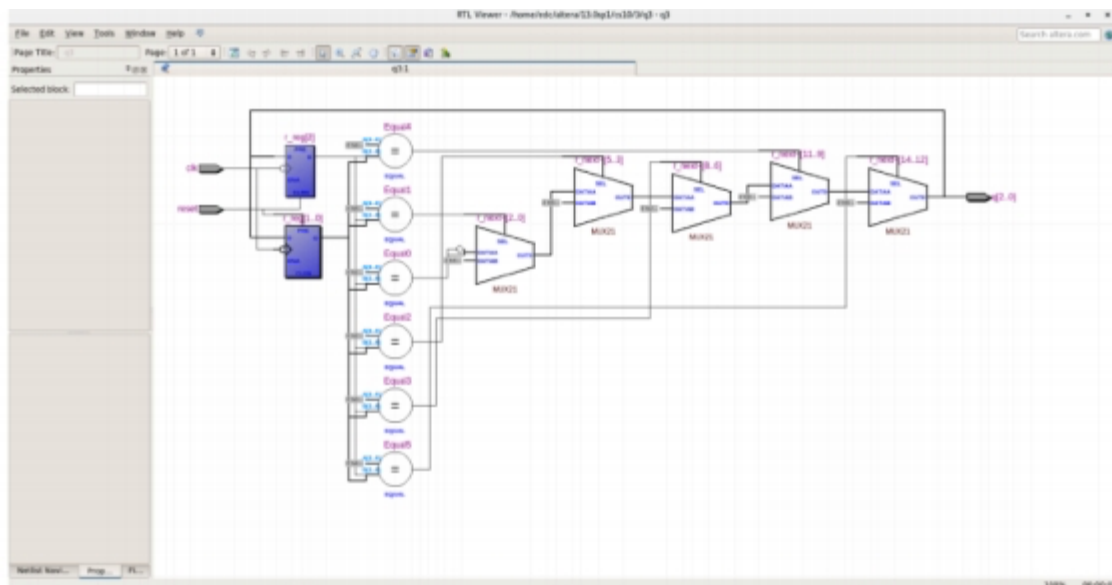

 

4. 3-bit Ring Counter

<i>Reset</i>	<i>Clock</i>	$Q_{(t-1)}$	$Q_{(t)}$
1	X	X	100
0	↓	100	010
0	↓	010	001
0	↓	001	100

code :

```


library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
6
entity q4 is
Port ( CLOCK : in STD_LOGIC;
RESET : in STD_LOGIC;
Q : out STD_LOGIC_VECTOR (2 downto 0));
end q4;
architecture Behavioral of q4 is
signal q_tmp: std_logic_vector(2 downto 0):= "000";
begin
process(CLOCK,RESET)
begin
if RESET = '1' then
q_tmp <= "001";

```

```

elsif falling_edge(CLOCK)
then
q_tmp(1) <= q_tmp(0);
q_tmp(2) <= q_tmp(1);
q_tmp(0) <= q_tmp(2);
end if;
end process;
Q <= q_tmp;
end Behavioral;

```

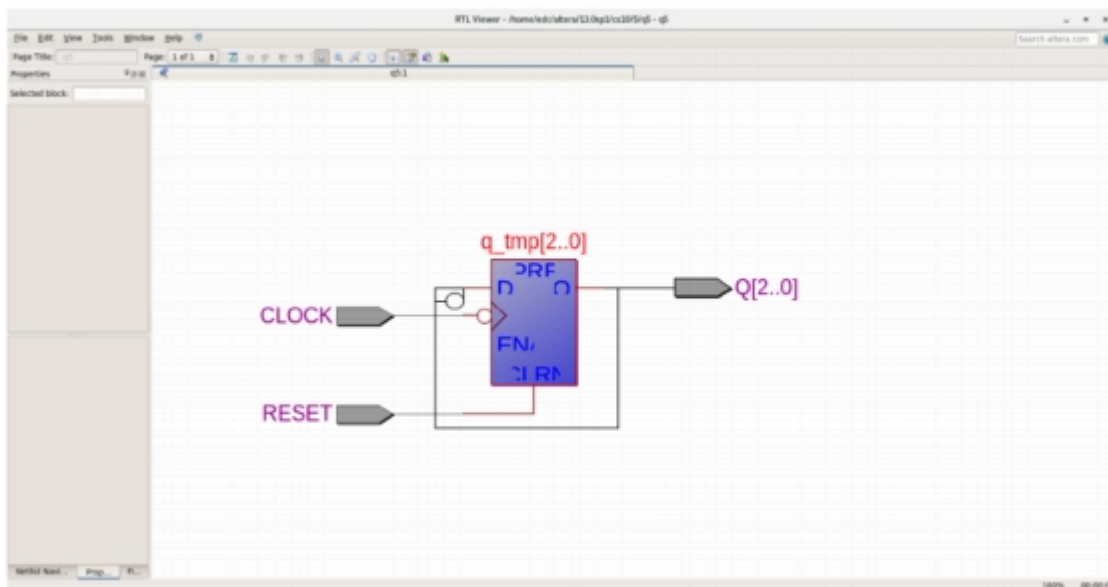

5. 3-bit Johnson Counter

<i>Reset</i>	<i>Clock</i>	$Q_{(t-1)}$	$Q_{(t)}$
1	X	X	000
0	↓	000	001
0	↓	001	011
0	↓	011	111
0	↓	111	110
0	↓	110	100
0	↓	100	000

code :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

entity **q5** is

```
Port ( CLOCK : in STD_LOGIC;
      RESET : in STD_LOGIC;
      Q : out STD_LOGIC_VECTOR (2 downto 0));
end q5;
```

architecture **Behavioral** of **q5** is

```
signal q_tmp: std_logic_vector(2 downto 0):= "000";
```

```
begin
```

```
process(CLOCK,RESET)
```

```
begin
```

```
if RESET = '1' then
```

```
    q_tmp <= "000";
```

```
elsif falling_edge(CLOCK) then
```


```
    q_tmp(1) <= q_tmp(0);
```

```
    q_tmp(2) <= q_tmp(1);
```

```
    q_tmp(0) <= not q_tmp(2);
```

```
end if;
```
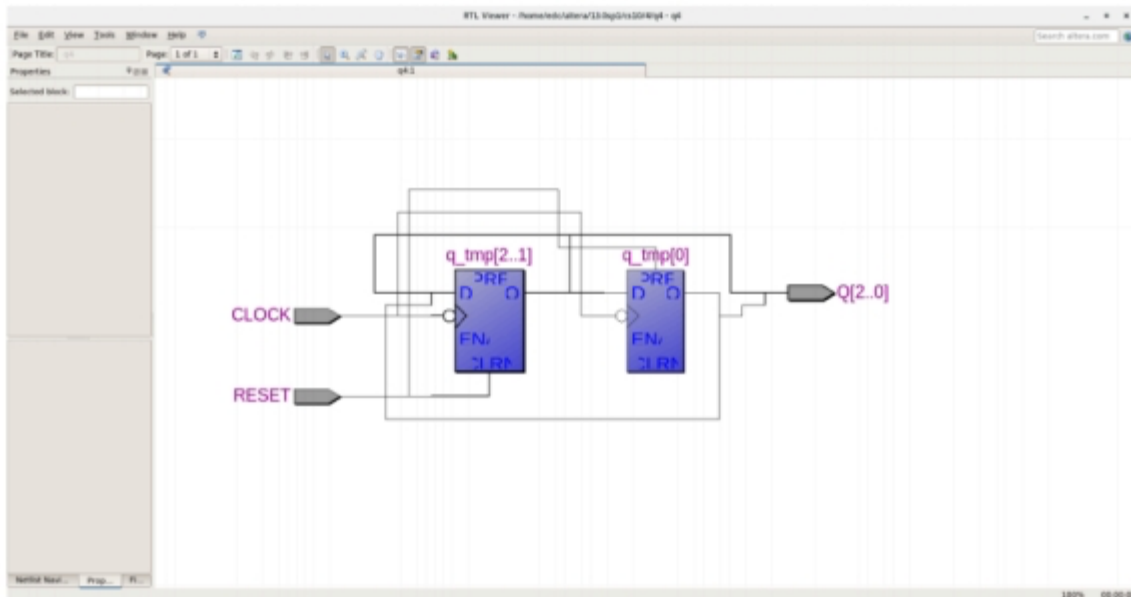
```
end process;  
Q <= q_tmp;  
end Behavioral;
```



Conclusion:

Writing VHDL codes and dumping those codes in CPLD boards for simulation of circuits for easier implementation of a combination of logic gates.

Thank You.