

# **CPLD MAX3000A**

D Flip-Flop and Shift Reg

4th April, 2023

VHDL Programming and CPLD Application the VHDL codes.

**Components used:**

Quartus software,CPLD Board and USB connector

**Summary:**

Using Quartus application to write the VHDL code for the given problems and dump the code the CPLD(blue board).

**1. DFF**

**Code:**

D Flip-Flop in Behavioural form:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity DFF_b is
port(d,clk,rst:in std_logic;
q:out std_logic
);
end DFF_b;

architecture Behavioral of DFF_b is
begin
process(rst,clk)
begin
if(rst= '1') then
q<='0';
elsif(clk'event and clk= '1') then
q<=d;
end if;
end process;
end Behavioral
```



### 3. Shift Reg

--MUX component:

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
entity mux is  
port(i0,i1, i2, i3, s0, s1: in std_logic;  
y: out std_logic);  
end mux;
```

architecture behavior of mux is

```
Begin  
c1: process (s0,s1)  
Begin  
if(s0= '0') then  
if(s1= '0') then  
y<=i0;  
else  
y<=i1;  
end if;  
else  
if(s1= '0') then  
y<=i2;  
else  
y<=i3;  
end if;  
end if;  
end process c1;  
end behavior;
```

-- D Flip-Flop component:

```
library IEEE;
```

```

use IEEE.STD_LOGIC_1164.ALL;
entity dff_shiftreg is
port(d,clk,rst:in std_logic;
q:out std_logic
);
end dff_shiftreg;

architecture Behavioral of dff_shiftreg is
begin
process(rst,clk)
begin
if(rst= '1') then
--IF RESET IS 1 THEN SET OUTPUT TO 0
q<='0';
elsif(clk'event and clk= '1') then
q<=d;
end if;
end process;
end Behavioral;

-- Universal Shift Register:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity shift-reg is
port(a1, a2, a3, sli, sri, m0, m1, clks, rsts: in std_logic;
o1, o2, o3: inout std_logic);
end shift-reg;

architecture structural of usr is
component dff_shiftreg is
port(d,clk,rst:in std_logic;
q:out std_logic);
end component;


```

```


component mux is
port(i0, i1, i2, i3, s0, s1: in std_logic;
y: out std_logic);
end component;

signal d1,d2,d3:std_logic;
begin
mux1: mux port map(i0=>a1, i1=>sli, i2=>o2, i3=>o1, s0=>m0,
s1=>m1, y=>d1);
mux2: mux port map(i0=>a2, i1=>o1, i2=>o3, i3=>o2, s0=>m0,
s1=>m1, y=>d2);
mux3: mux port map(i0=>a3, i1=>o2, i2=>sri, i3=>o3, s0=>m0,
s1=>m1, y=>d3);
ff1: dff_shiftreg port map(d=>d1, clk=>clks, rst=>rsts, q=>o1);
ff2: dff_shiftreg port map(d=>d2, clk=>clks, rst=>rsts, q=>o2);
ff3: dff_shiftreg port map(d=>d3, clk=>clks, rst=>rsts, q=>o3);
end structural;

```

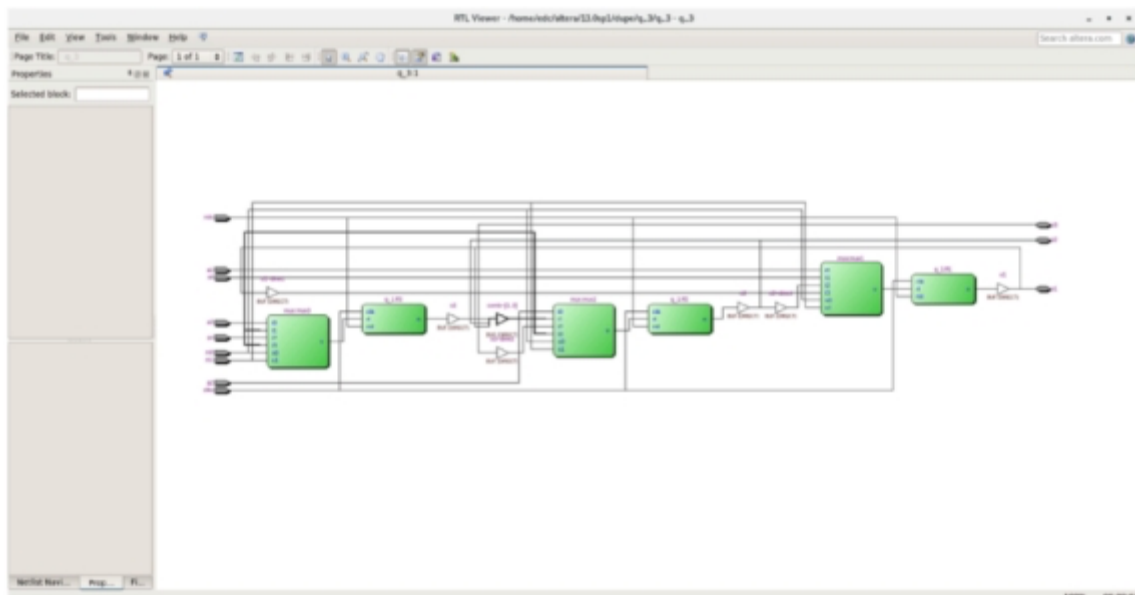

### **Circuit Snapshots:**

 

### **Conclusion:**

Writing VHDL codes and dumping those codes in CPLD boards for simulation of circuits for easier implementation of a combination of logic gates.

# Thank You.